

Table 5.11-2 Thévenin and Norton Equivalent Circuits

ORIGINAL CIRCUIT	THÉVENIN CIRCUIT	NORTON EQUIVALENT CIRCUIT

## PROBLEMS

## Section 5.3 Source Transformations

**P 5.3-1** The circuit shown in Figure P 5.3-1a has been divided into two parts. The circuit shown in Figure P 5.3-1b was obtained by simplifying the part to the right of the terminals using source transformations. The part of the circuit to the left of the terminals was not changed.

(a) Determine the values of  $R_t$  and  $v_t$  in Figure P 5.3-1b.

(b) Determine the values of the current  $i$  and the voltage  $v$  in Figure P 5.3-1b. The circuit in Figure P 5.3-1b is equivalent to the circuit in Figure P 5.3-1a. Consequently, the current  $i$  and the voltage  $v$  in Figure P 5.3-1a have the same values as do the current  $i$  and the voltage  $v$  in Figure P 5.3-1b.

(c) Determine the value of the current  $i_a$  in Figure P 5.3-1a.

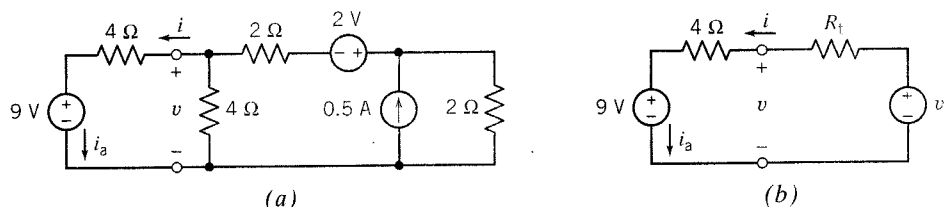


FIGURE P 5.3-1

**P 5.3-2** Consider the circuit of Figure P 5.3-2. Find  $i_a$  by simplifying the circuit (using source transformations) to a single-loop circuit so that you need to write only one KVL equation to find  $i_a$ .

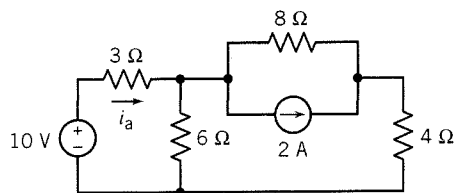


FIGURE P 5.3-2

**P 5.3-3** Find  $v_o$  using source transformations if  $i = 5/2$  A in the circuit shown in Figure P 5.3-3.

**Hint:** Reduce the circuit to a single mesh that contains the voltage source labeled  $v_o$ .

**Answer:**  $v_o = 28$  V

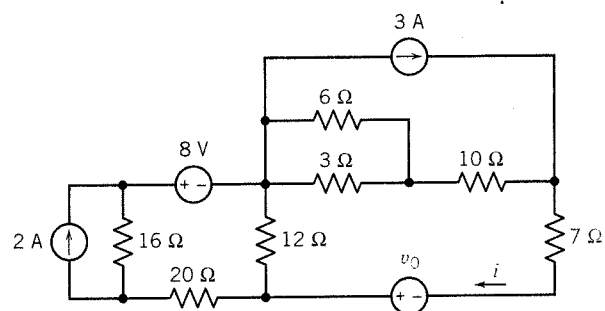


FIGURE P 5.3-3

**P 5.3-4** Determine the value of the current  $i_a$  in the circuit shown in Figure P 5.3-4.

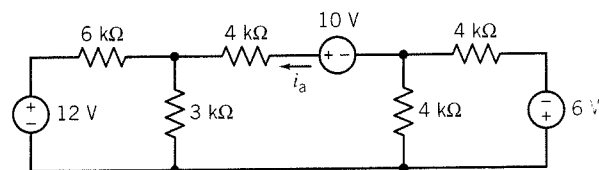


FIGURE P 5.3-4